



LAB 3: Simple Finite State Machine

Nate Lannan

Oklahoma State University

Electrical and Computer Engineering Department

Stillwater, OK 74078 USA

nate.lannan@okstate.edu


Objective

- This lab has several key objectives:
 - See what sequential logic and how to implement it in HDL.
 - Learn how HDL implementations are different than their design on paper.
 - Understand the difference between clock within digital logic and how it differs from real time.
 - Implement a simple Finite State Machine (FSM)
 - Thunderbird FSM.
 - Add hazards
 - Understand debugging of FSMs


FSMs

- **Next state** determined by current state and inputs
- Two types of finite state machines differ in **output logic**:
 - **Moore FSM**: outputs depend only on current state
 - **Mealy FSM**: outputs depend on current state *and* inputs


Moore FSM

 

Mealy FSM

 


Implementation

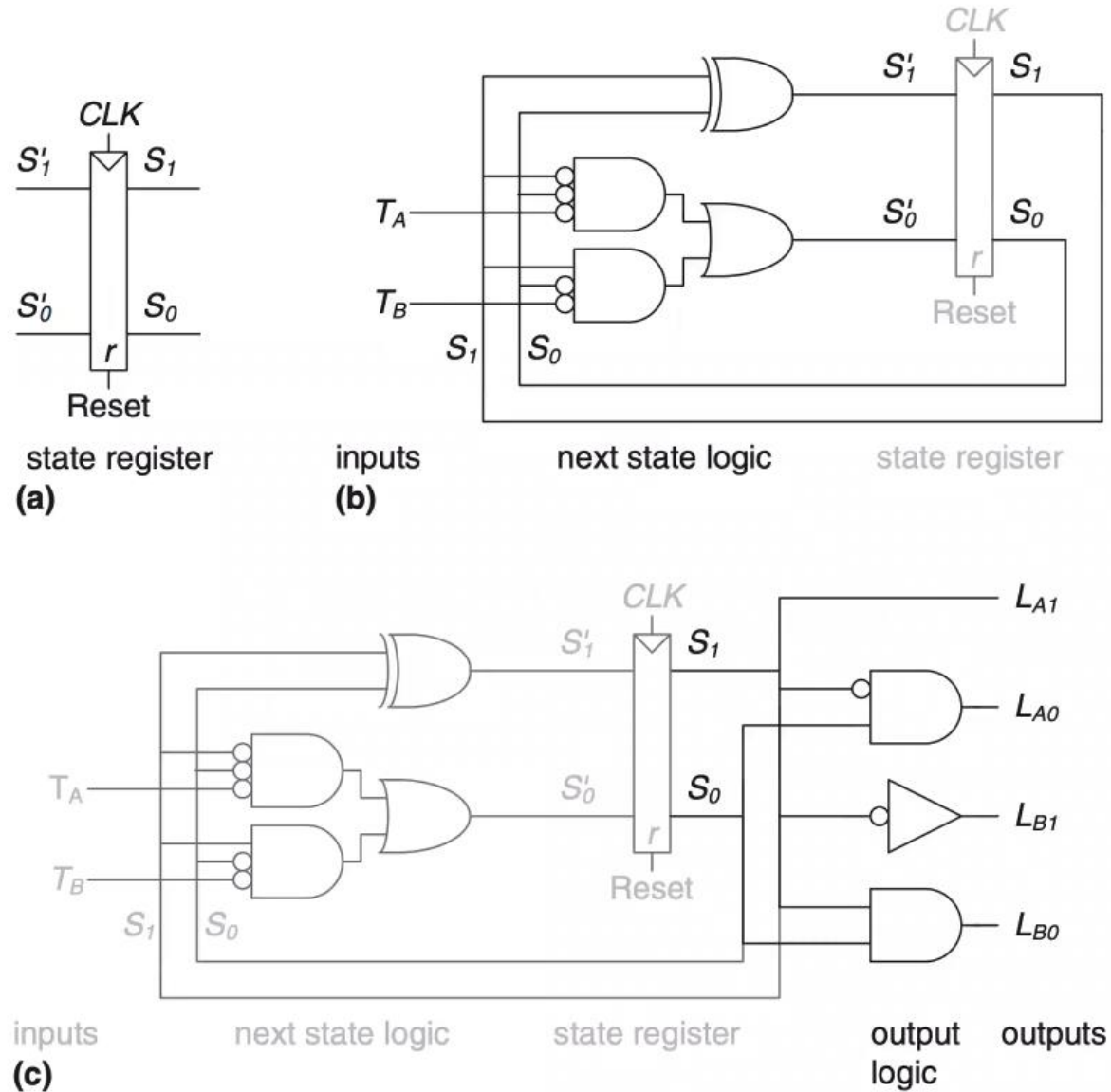

How do we implement in HDL

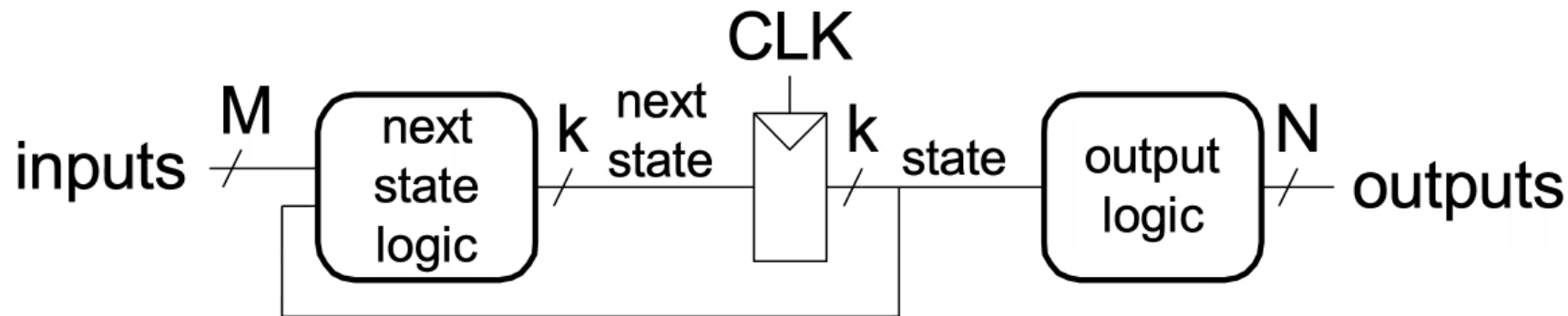- **Three blocks:**
 - next state logic
 - state register
 - output logic
- FSMs in HDL should always have a next-state and state-register section.
- The output logic can be integrated into the state next-state section, if needed.
 - That is, either is acceptable but having three sections saves work as we will see!



FSM Implementation in SV


```
module divideby3FSM (input  logic clk,
                    input  logic reset,
                    output logic q);

    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype [1:0] state, nextstate;

    // state register
    always_ff @ (posedge clk, posedge reset)
        if (~reset) state <= S0;
        else       state <= nextstate;


    // next state logic
    always_comb
        case (state)
            S0:
                begin
                    nextstate = S1;
                    q = 1'b1;
                end
            S1:
                begin
                    nextstate = S2;
                    q = 1'b0;
                end
            S2:
                begin
                    nextstate = S0;
                    q = 1'b0;
                end
            default:
                begin
                    nextstate = S0;
                    q = 1'b0;
                end
        endcase
endmodule
```

What are we implementing?

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

 Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



[Wakerly]

<https://youtu.be/5azgaPDvPDk>

Seems rather straightforward?

- Yes, it is very simple if you follow the SV HDL coding methodology.
- What's the challenge?
 - The challenge is that the clock on the DSDB board operates so much faster than what our eyes see!
 - We need to slow the clock down in order to even see things!
- We use a clock to synchronize, so you can always slow things down in two ways:
 - Use a clock enabler that activates only once per so many iterations.
 - The other option, which we are using here, is a clock divider like the design we created in class but with a counter.


Clock Divider

```
module clk_div (input logic clk, input logic rst, output logic clk_en);

    logic [23:0] clk_count;

    always_ff @(posedge clk)
    //posedge defines a rising edge (transition from 0 to 1)
    begin
        if (rst)
            clk_count <= 24'h0;
        else
            clk_count <= clk_count + 1;
        end
    assign clk_en = clk_count[23];
endmodule
```


Basic Clock Divider Architecture

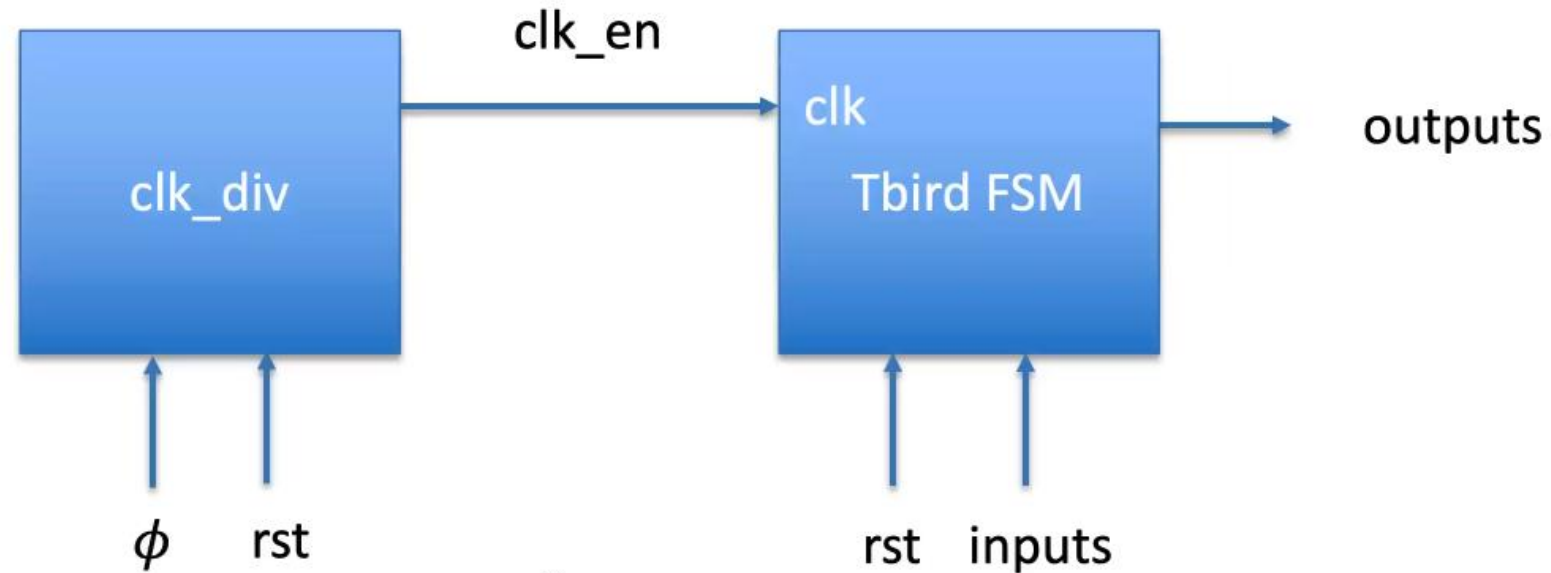


Hints

- Use the LEDs, 7-segment display, and other items on your DSDB to help you.
- Always simulate with the testbench before you begin implementing!!!
 - Do not even attempt the implementation without trying to completely verify your state machine in a testbench.
 - FSMs are notoriously more difficult than combinational logic in that the output is now comprised of inputs + current state which leaves so many more possible combinations that can lead to failure.
- Use the `clk_en` output from the clock divider to clock your FSM.
 - Play around with the counter to change the time the lights blink.
- Use your GUI to help you debug things
 - Always output `CURRENT_STATE` and `NEXT_STATE` to your GUI to see what state you are in to see what is happening.

MGC ModelSim Wave Window

 

MGC ModelSim Wave Window

 

DOT files

- Drawing your FSM might be difficult.
- I have provided a DOT file in the repository for graphviz as its easy to use.
- Search “graphviz online”
 - Let’s try...

Conclusion

- FSMs are fun but good methodologies for implementing and debugging HDL are essential to making these designs work.
- Almost every digital design uses a FSM to control its behavior
 - It is important you understand how to design FSMs and implement them.
 - Good combinational logic understanding is essential to making FSMs work properly.
 - Design of FSMs on paper differs from what you implement in a HDL but everything always starts with the state-transition table (do not forget to make one for this laboratory).